SEL0414 - Sistemas Digitais Resolução Lista 7 - Codificadores e Decodificadores


$'COST = \$72' \Rightarrow (434F53543D243732)_h$
02
$(010100110101010001001111101010000)_b = (53544F50)_h = 'STOP'$
03
a.
Codificador
b.
Codificador
c.
Decodificador


01


 $\mathbf{d}.$


 ${\bf Decodificador}$


A	B	10	D	SAIDA	A	B	C	D	SATDA ATIVA
0	0	0	0	50	0	Δ	0	0	Sy
0	0	0	1	5,	0	1	0	1	Se
0	0	7	0	Sz	0	1	1	0	8
0	0	1	1	53	0	_1	1	١	54
	-			7,5-1			-		
A	B	C	D	SAT PA ATIVA	A	B	C	D	SATRA ATIVA
A	B 0	0	DO		A	8	0	DO	SO FRA ATIVA
		0 0		ATIVA	-	-			ATIVA
Δ	0		0	S8	1	-			ATIVA

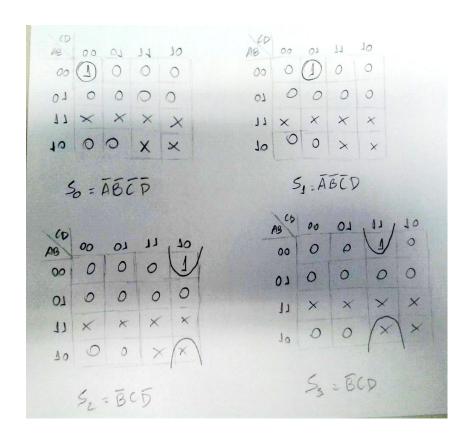


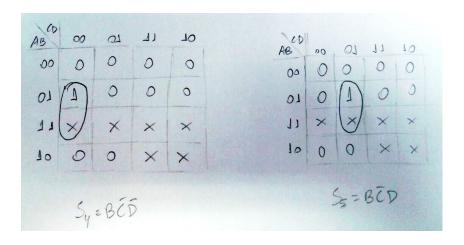

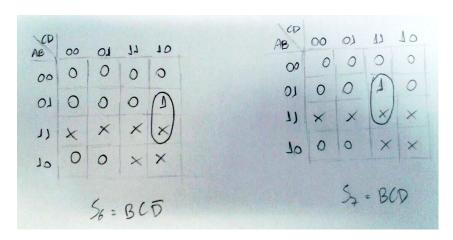


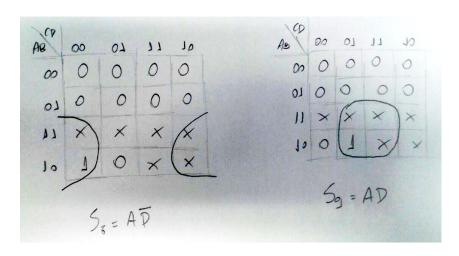

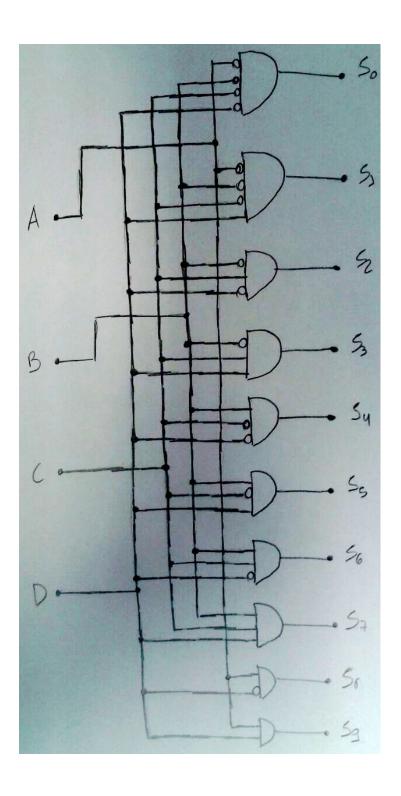


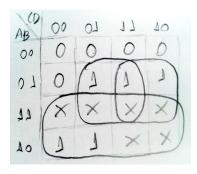


 $S_3 = A + BD + BC$

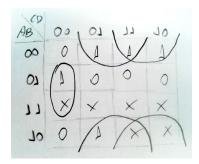

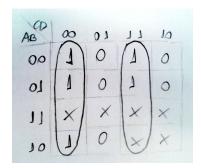
 $S_2 = B\overline{C}\overline{D} + \overline{B}D + \overline{B}C = B\overline{C}\overline{D} + \overline{B}(C+D) = B\overline{C} + \overline{D} + \overline{B}(C+D) = B \oplus (C+D)$




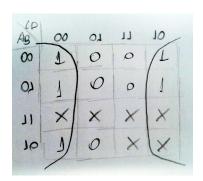
$$S_1 = \overline{C}\overline{D} + CD = \overline{C \oplus D}$$




$$S_0 = \overline{D}$$

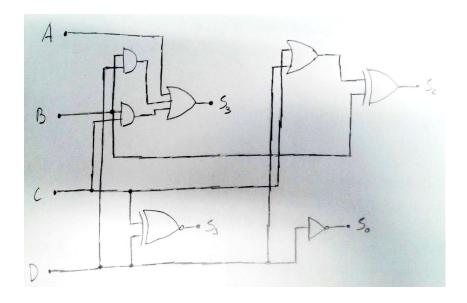

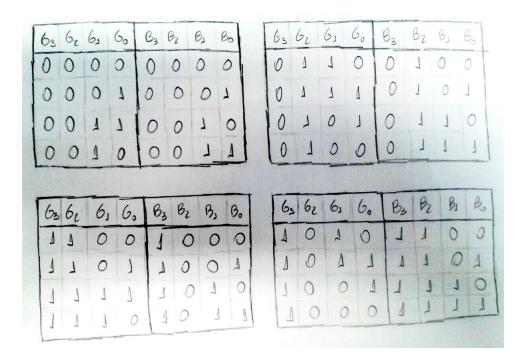


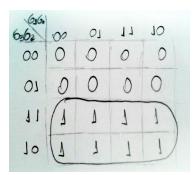


$$B_3 = G_3$$

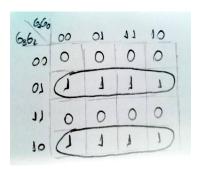

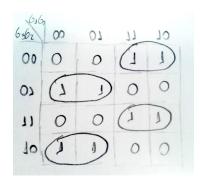
$$B_2 = \overline{G_3}G_2 + G_3\overline{G_2} = G_3 \oplus G_2$$


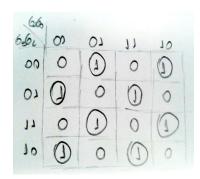
$$B_1 = \overline{G_3}\overline{G_2}G_1 + \overline{G_3}G_2\overline{G_1} + G_3G_2G_1 + G_3\overline{G_2}\overline{G_1} = \overline{G_3}(G_2 \oplus G_1) + G_3(\overline{G_2 \oplus G_1}) = G_3 \oplus G_2 \oplus G_1$$



 $B_0 = \overline{G_3}\overline{G_2}\overline{G_1}G_0 + \overline{G_3}\overline{G_2}G_1\overline{G_0} + \overline{G_3}G_2\overline{G_1}\overline{G_0} + \overline{G_3}G_2\overline{G_1}G_0 + \overline{G_3}G_2G_1\overline{G_0} + \overline{G_3}G_2\overline{G_1}G_0 + G_3\overline{G_2}G_1\overline{G_0} + G_3\overline{G_2}\overline{G_1}G_0 + G_3\overline{G_2}G_1\overline{G_0} + G_3\overline{G_2}G_1\overline$

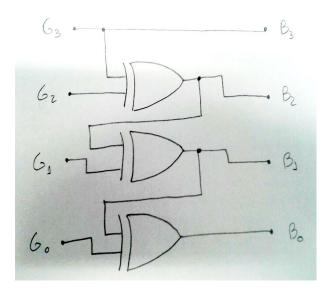

A solução dessa questão se encontra a partir do slide 23 da Aula 7.